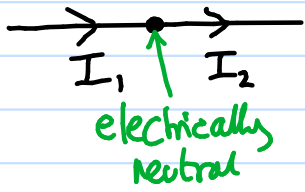



Circuit rules

Kirchhoff's first law : $\sum I = 0$
(Kirchhoff's current law) - KCL



$$I_1 = I_2$$

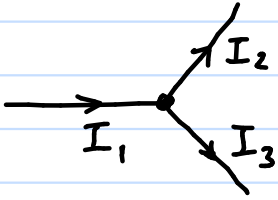because of conservation of charge
and charge does not accumulate
at the junction ($I = \frac{Q}{t}$)



$$I_1 = I_2 + I_3$$



lets say current into a junction is +ve
and current out of a junction is -ve.

$$\sum I = I_1 + I_2 + I_3 = 0$$

+ve -ve -ve

Kirchhoff's second law :
(Kirchhoff's voltage law) - KVL
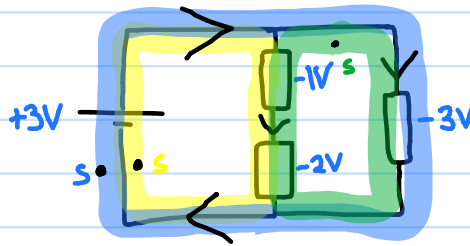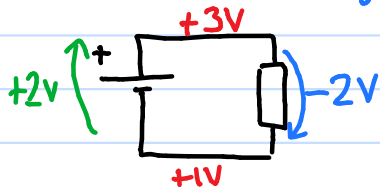
$$\sum V = 0 \quad (\text{around a circuit loop})$$




$$3 - 1 - 2 = 0$$

$$3 - 3 = 0$$

$$-3 - (-2) - (-1) = 0$$

Conservation of energy
because ($V = \frac{W}{Q}$)

Example :

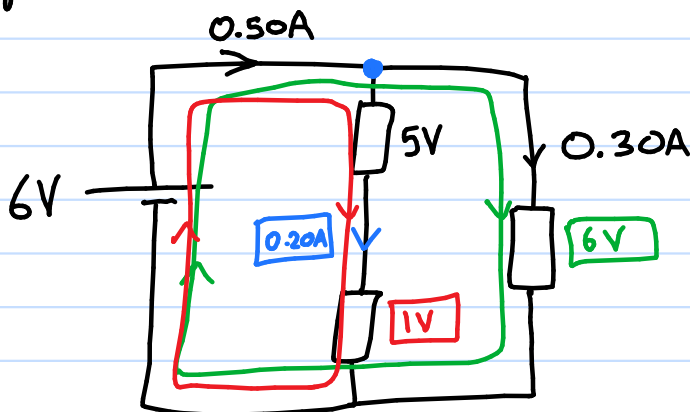

$$\text{KI: } 0.50 - 0.30 - I = 0$$
$$I = 0.20$$

$$\text{KII: } 6 - V = 0$$
$$V = 6$$

$$\text{KII: } 6 - 5 - V = 0$$
$$V = 1$$

More about resistance

$$P = VI \quad V = IR$$

$$I = \frac{V}{R}$$

$$P = I^2 R$$


$$P = \frac{V^2}{R}$$

$$P \propto R \quad \text{if } I \text{ is constant}$$


$$P \propto \frac{1}{R} \quad \text{if } V \text{ is constant}$$

- Electromotive force, emf $\mathcal{E}$ is p.d. gained from power supply

Simplifying circuits can be helpful

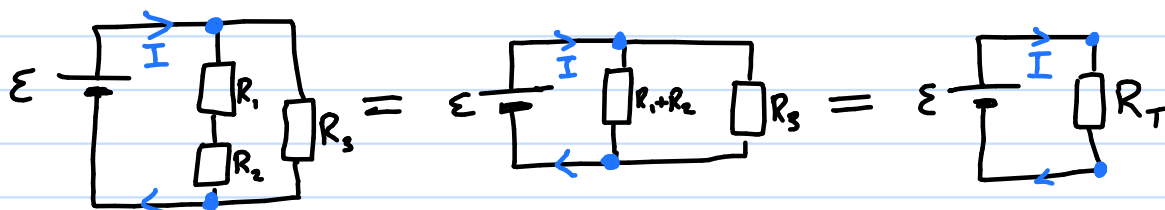

Resistors in series :

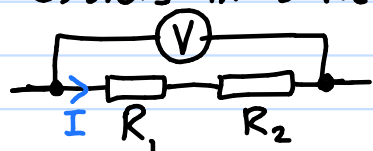


$$KI : V_1 + V_2 = V \quad \text{use } V = IR$$

$$\cancel{I}R_1 + \cancel{I}R_2 = \cancel{I}R_T$$

$$R_T = R_1 + R_2$$

$$R_T = \sum_{n=1}^N R_n$$

Resistors in parallel :

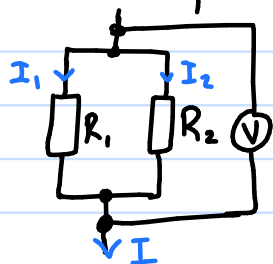


$$KI : I_1 + I_2 = I \quad \text{use } V = IR \quad I = \frac{V}{R}$$

$$\cancel{\frac{V}{R_1}} + \cancel{\frac{V}{R_2}} = \cancel{\frac{V}{R_T}} \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$R_T = \left[\sum_{n=1}^N \frac{1}{R_n} \right]^{-1}$$

Example :

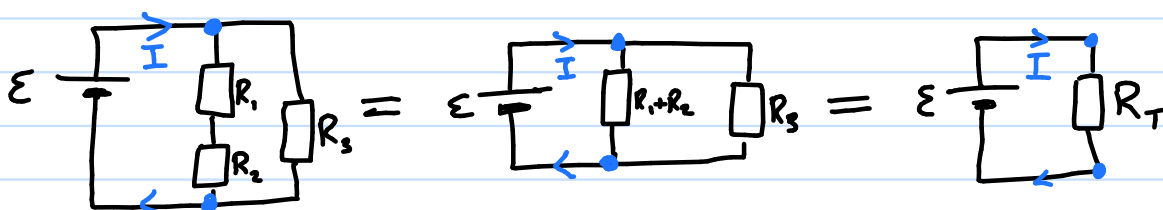


$$R_T = \left(\frac{1}{R_1 + R_2} + \frac{1}{R_3} \right)^{-1} = \left[(R_1 + R_2)^{-1} + R_3^{-1} \right]^{-1}$$

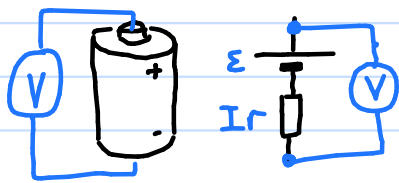Electromotive force and internal resistance





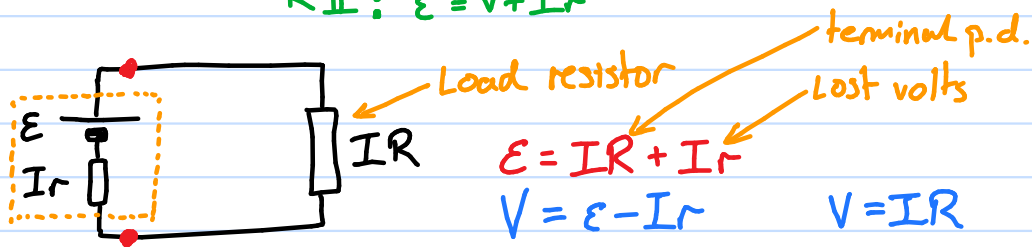V is the terminal p.d.
 r is the internal resistance of the supply
 KII: $\epsilon = V + Ir$



EMF ϵ will equal terminal p.d. when $I = 0$

Measure internal resistance

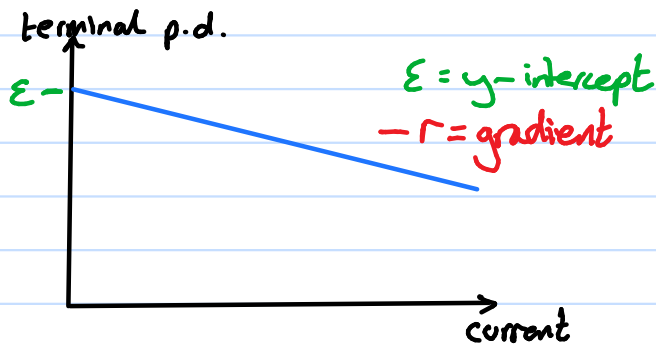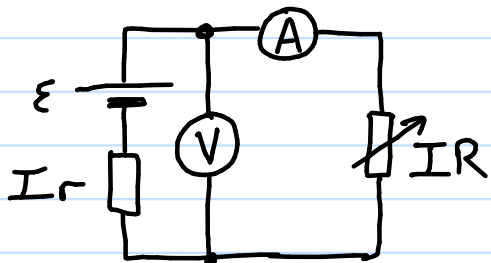

$V = \epsilon - Ir$
 terminal p.d. ϵ lost volts

$y = mx + c$
 $V = -rI + \epsilon$

Power

$P = I^2 R$


- so does P increase as R increases? If V was constant, yes!
- I decreases as R increases, so does P decrease as R increases?
- We need to include R and r in our calculation of power delivered to load resistor R

$\epsilon = Ir + IR = I(R+r) \Rightarrow I = \frac{\epsilon}{R+r}$ substitute into $P = I^2 R$

$P = \epsilon^2 \frac{R}{(R+r)^2}$

for small R , $P \propto R$
 for big R , $P \propto 1/R$



power delivered to R

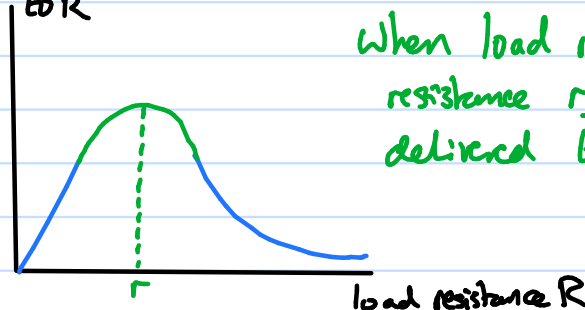


When load resistance $R =$ internal resistance r , maximum power is delivered to R

More circuit calculations

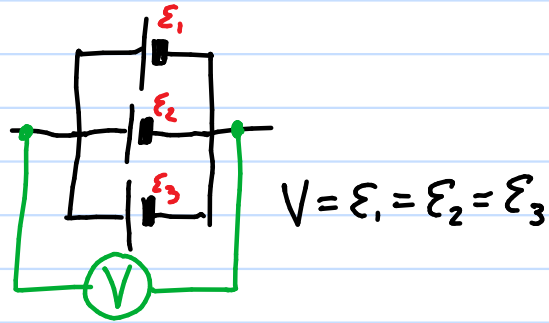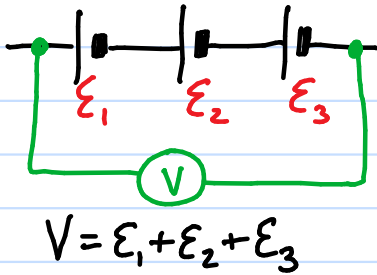
If cells did not have internal resistance?



If cells do have internal resistance?

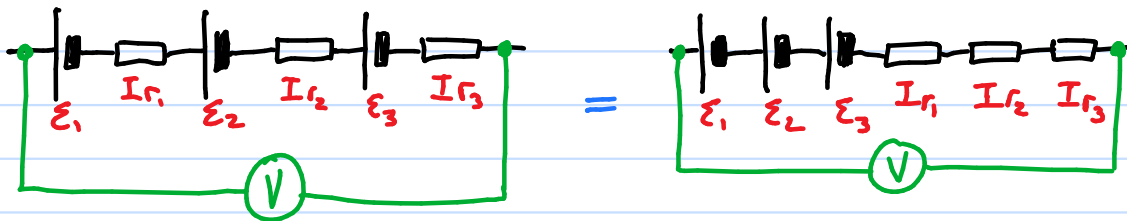

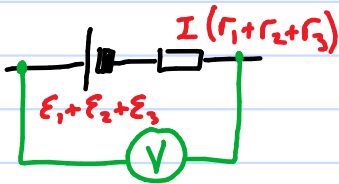
$$V = \epsilon_1 - I r_1 + \epsilon_2 - I r_2 + \epsilon_3 - I r_3 = V = \epsilon_1 + \epsilon_2 + \epsilon_3 - I r_1 - I r_2 - I r_3$$



In series, we can simply add together emfs, and combine internal resistances into a single resistor.

In parallel

Assume identical cells

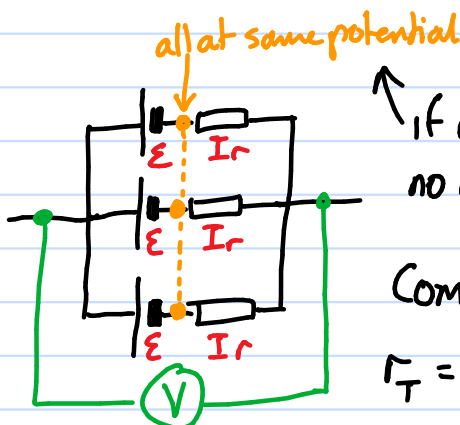

Combined internal resistance

$$r_T = \left[\sum_{n=1}^N r_n^{-1} \right]^{-1} \text{ in this case } r_T = \frac{1}{3} r$$


$$V = \epsilon - \frac{1}{3} I r$$

Diodes

forward bias


Treat diodes like sources of emf in reverse

Drop 0.7V across diode

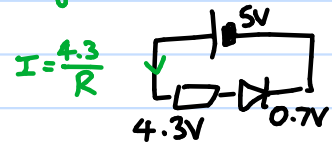


Reverse bias

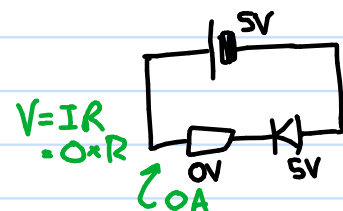Treat like open circuit.
i.e. infinite resistance



The potential divider

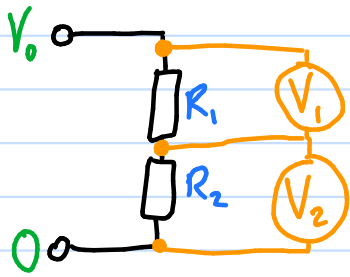

• Because of KI, both resistors have same current passing through through

$$V = IR \quad V_1 = I_1 R_1 \quad V_2 = I_2 R_2 \quad V_0 = I_0 R_0$$

$$\begin{aligned} KI & \Rightarrow I_1 = I_2 = I_0 \\ KI & \Rightarrow V_1 + V_2 = V_0 \end{aligned}$$

Combining resistors, $R_0 = R_1 + R_2$

$$I_0 = I_1 = I_2 \Rightarrow \frac{V_1}{R_1} = \frac{V_2}{R_2} = \frac{V_0}{R_0}$$


$$\frac{V_1}{R_1} = \frac{V_0}{R_1 + R_2} \Rightarrow \frac{V_1}{V_0} = \frac{R_1}{R_1 + R_2}$$

$$\frac{V_2}{R_2} = \frac{V_0}{R_1 + R_2} \Rightarrow \frac{V_2}{V_0} = \frac{R_2}{R_1 + R_2}$$

The share of p.d. across a resistor in a potential divider circuit is equal to its share of the resistance.

$$V_1 = V_0 \left(\frac{R_1}{R_1 + R_2} \right) \quad V_2 = V_0 \left(\frac{R_2}{R_1 + R_2} \right)$$

Example

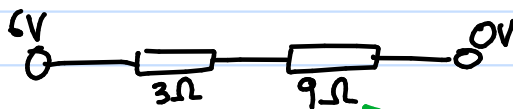

$\frac{1}{4}$ of the resistance so has p.d. of $\frac{1}{4} \times 6V = 1.5V$

$\frac{3}{4}$ of the resistance so has p.d. of $\frac{3}{4} \times 6V = 4.5V$


$$I = \frac{6}{3+9} = 0.50A$$

$$V = IR$$


$$V_3 = 0.50 \times 3 = 1.5V$$

$$V_9 = 0.50 \times 9 = 4.5V$$

Potentiometer

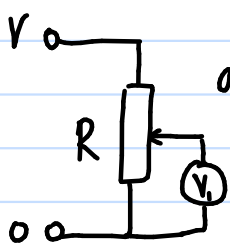


are just like

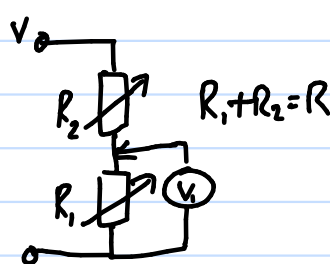

Sensing circuits

LDRs, resistance decreases as light intensity increases

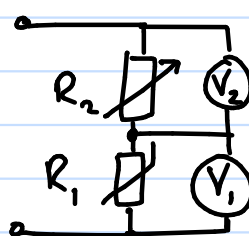Thermistors, resistance decreases as temperature increases



- As temperature increases
- R_1 decreases
- V_1 decrease proportionally to the share of resistance
- V_2 increase!